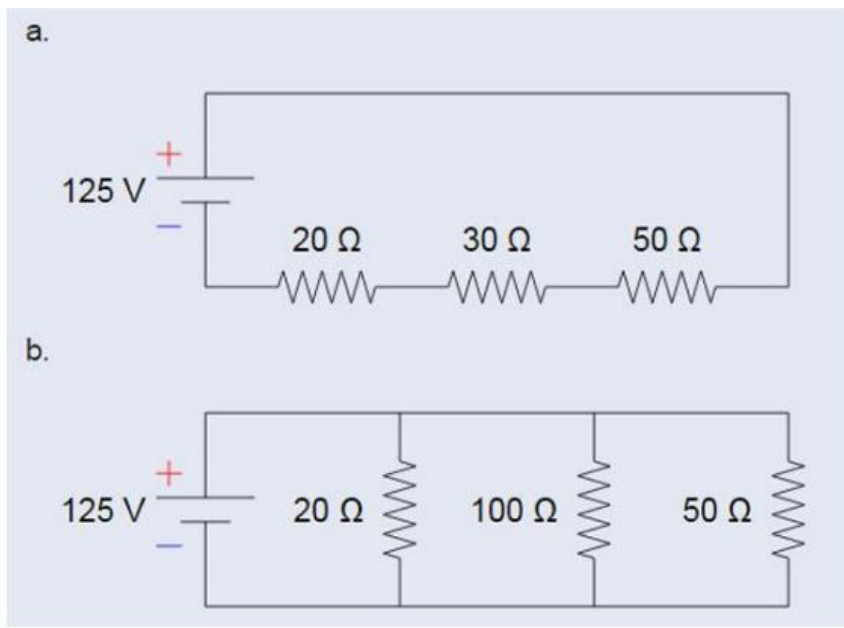


IOT assignment 2



For each of these circuits:

- Calculate the total resistance in ohms,
 - $20 + 30 + 50 = 100\text{ohms}$
 - $1/20 + 1/100 + 1/50 = 12.5\text{ohms}$
- Calculate the total current from the power supply,
 $V = IR$, SO $I = V/R$
 - $125/100 = 1.25\text{A}$
 - $125/12.5 = 10\text{A}$
- Calculate the current through each resistor
 - 1.25A since current in a series circuit is the same everywhere
 - Voltage is the same, so $I = V/R$
 - 1- $125/20 = 6.25\text{A}$
 - 2- $125/100 = 1.25\text{A}$
 - 3- $125/50 = 2.5\text{A}$
- Calculate the Voltage drop through each resistor
 - $V = IR$
 - 1- $1.25 \times 20 = 25\text{ V}$
 - 2- $1.25 \times 30 = 37.5\text{ V}$
 - 3- $1.25 \times 50 = 62.5\text{ V}$
 - Voltage is the same all across so 125V
- Calculate the Power dissipated through each resistor (use Watt's Law: Power = Voltage * Current)
 - $P = VI$
 - 1- $25 \times 1.25 = 31.25\text{ W}$
 - 2- $37.5 \times 1.25 = 46.875\text{ W}$
 - 3- $62.5 \times 1.25 = 78.125\text{ W}$

b.

i. $1 - 125 \times 6.25 = 781.25 \text{ W}$

ii. $2 - 125 \times 1.25 = 156.25 \text{ W}$

iii. $3 - 125 \times 2.5 = 312.5 \text{ W}$